

Q1) cylindrical tube of radius 2mm and length 7 cm have atoms density $32 \times 10^{20} \text{ m}^{-3}$ to produce N-type semiconductor calculate

- 1- Conductivity and resistivity
- 2- Resistance of tube
- 3- Calculate new tube length to produce resistance 50Ω

(hint: $e=1.6 \times 10^{-19}$, $\mu_e=0.36 \text{ m}^2/(\text{v}.\text{sec})$)

Q2) cylindrical tube of radius 3mm and length 320mm have atoms density $40 \times 10^{19} \text{ m}^{-3}$ to produce P-type semiconductor calculate (8 degree)

- 1- Conductivity and resistivity
- 2- Resistance of tube
- 3- Calculate new tube radius to produce resistance 60Ω

(hint: $e=1.6 \times 10^{-19}$, $\mu_h=0.18 \text{ m}^2/(\text{v}.\text{sec})$)

Q3) Determine the resistance of a silicon sample having an area of 1 cm^2 and a length of 3 cm for atomic density $32 \times 10^{20} \text{ m}^{-3}$ of N-type semiconductor.

Q4) Repeat part (Q3) if the length is 1 cm and the area 4 cm^2 .

Q5). Describe the difference between n-type and p-type semiconductor materials.

Q6). Describe the difference between donor and acceptor impurities.

Q7). Describe the conditions established by forward- and reverse-bias conditions on a p-n junction diode and how the resulting current is affected.


Q8). Describe how you will remember the forward- and reverse-bias states of the p-n junction diode.

Q9). Determine the diode current at 30°C (room temperature) for a silicon diode with $I_s= 50 \text{ nA}$ and an applied forward bias of 0.6 V.


Q10). Repeat (Q9) for $T = 100^\circ\text{C}$.

Q11). Determine the diode current at room temperature for a silicon diode with $I_s= 0.1 \text{ A}$ at a reverse-bias potential of 10 V.

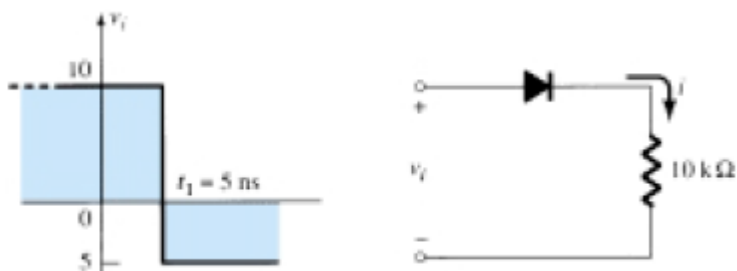
Q12). Sketch the waveform for (i and V_o) of the cct. shown below



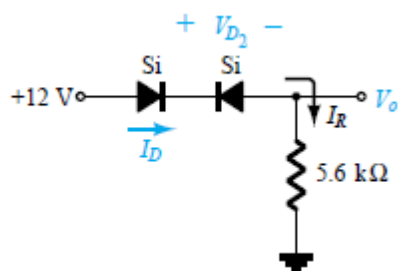
Q13). Determine I_D , V_{D2} , and V_o for the circuit shown below if ($V_o = 0.6$ v and $R_D=100$ ohm)



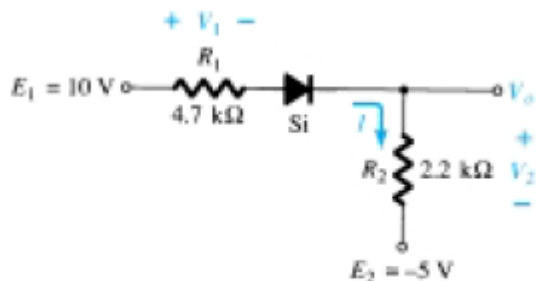
Q14) Determine I, V_1 , V_2 , and V_o for the cct. shown below if ($V_o = 0.6$ v and $R_D=100$ ohm)



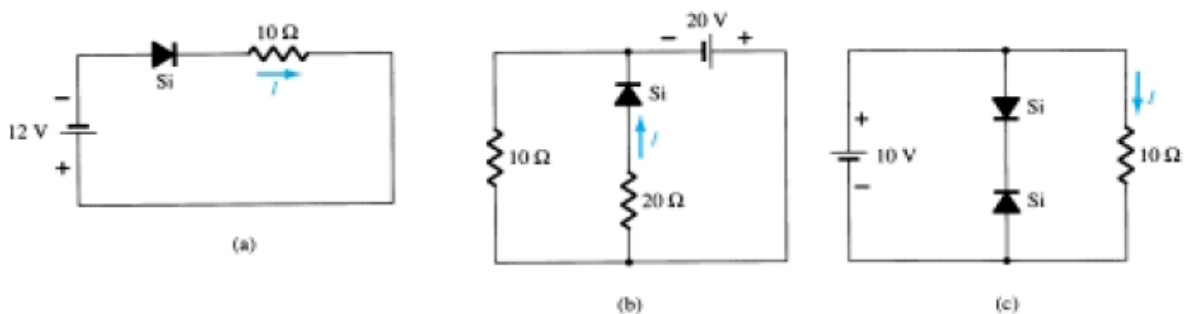
Q15) Determine the current I for each of the three ccts. ($V_o = 0$ v and $R_D=100$ ohm)



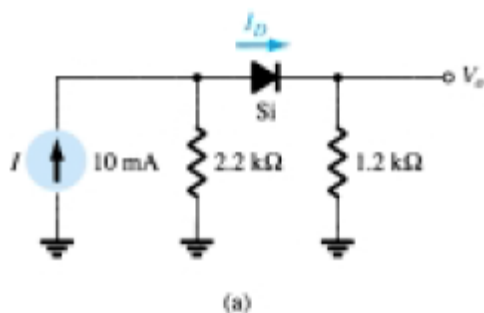
Q16) Determine V_o and I_D for the cct. shown below ($V_o = 0$ v and $R_D=400$ ohm)



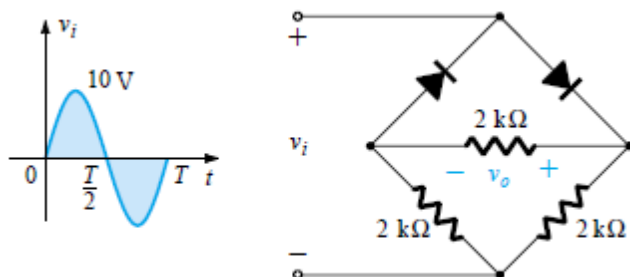Q17) Determine the output waveform for the cct. shown below and calculate the output required PIV of each diode



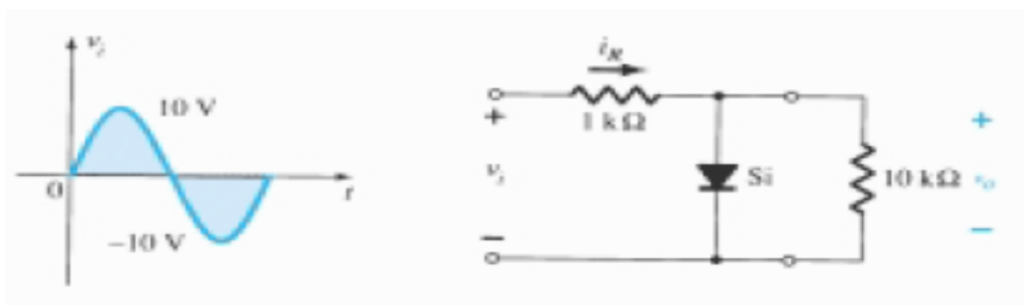Q18) For the cct. shown below , sketch v_o and i_R .




Q19) A FWR center tap transformer with a 120-V sinusoidal input and transformer ratio 10:1 has a load resistor of 1000 ohm.

- If silicon diodes are employed, what is the dc voltage available at the load?
- Determine the required PIV rating of each diode.
- Find the maximum current through each diode during conduction.
- What is the DC power and ac power of the output wave?

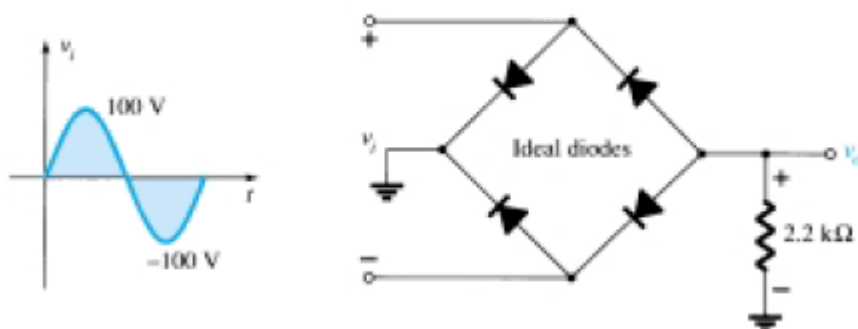
Q20) A FWR shown below find

- If silicon diodes are employed, what is the dc voltage available at the load?
- Determine the required PIV rating of each diode.
- Find the maximum current through each diode during conduction.
- What is the DC power and ac power of the output wave?




Q21) (a) For the Zener diode cct. shown below, determine V_L , V_R , I_Z , and P_Z .

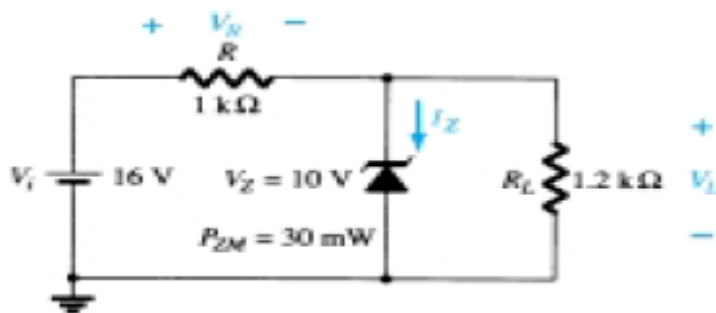(b) Repeat part (a) with $R_L = 3 \text{ k}\Omega$.




Q22) (a) For the cct. shown below determine the range of R_L and I_L .

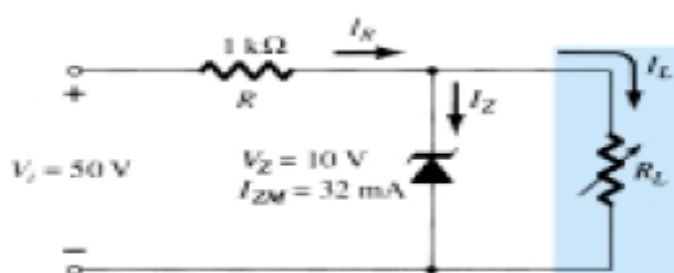
b) Determine the maximum zener diode power.



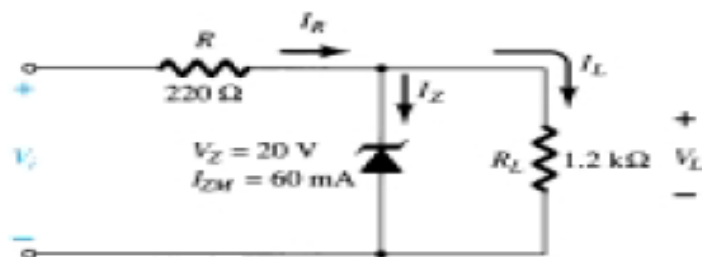
Q23) Determine the range of values of V_i that will maintain the Zener diode for the cct. shown below in the “on” state.



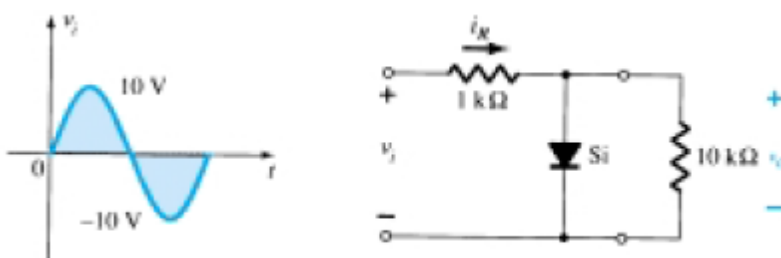Q24) For the cct. shown below sketch v_o and i_R .




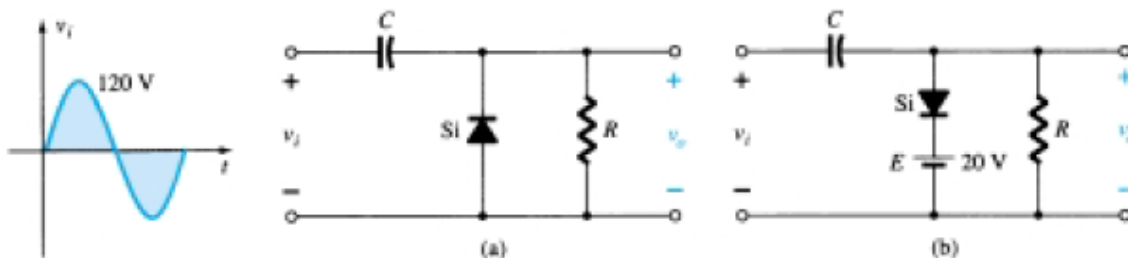Q25) Sketch v_o for each ccts. Shown below for the input shown.



Q26) Design a voltage regulator that will maintain an output voltage of 20 V across a 1500 ohm load with an input 50 V. That is, determine the proper value of R_s and the maximum current I_Z .

Q27) Design the cct. shown below to maintain $V_L = 12$ V for a load variation (I_L) from 0 to 200 mA. That is, determine R_s , V_Z and P_{Zmax} for the Zener diode.

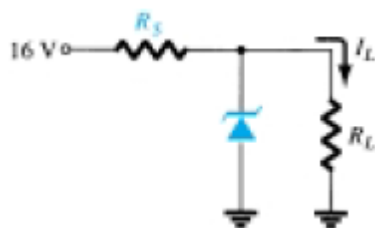

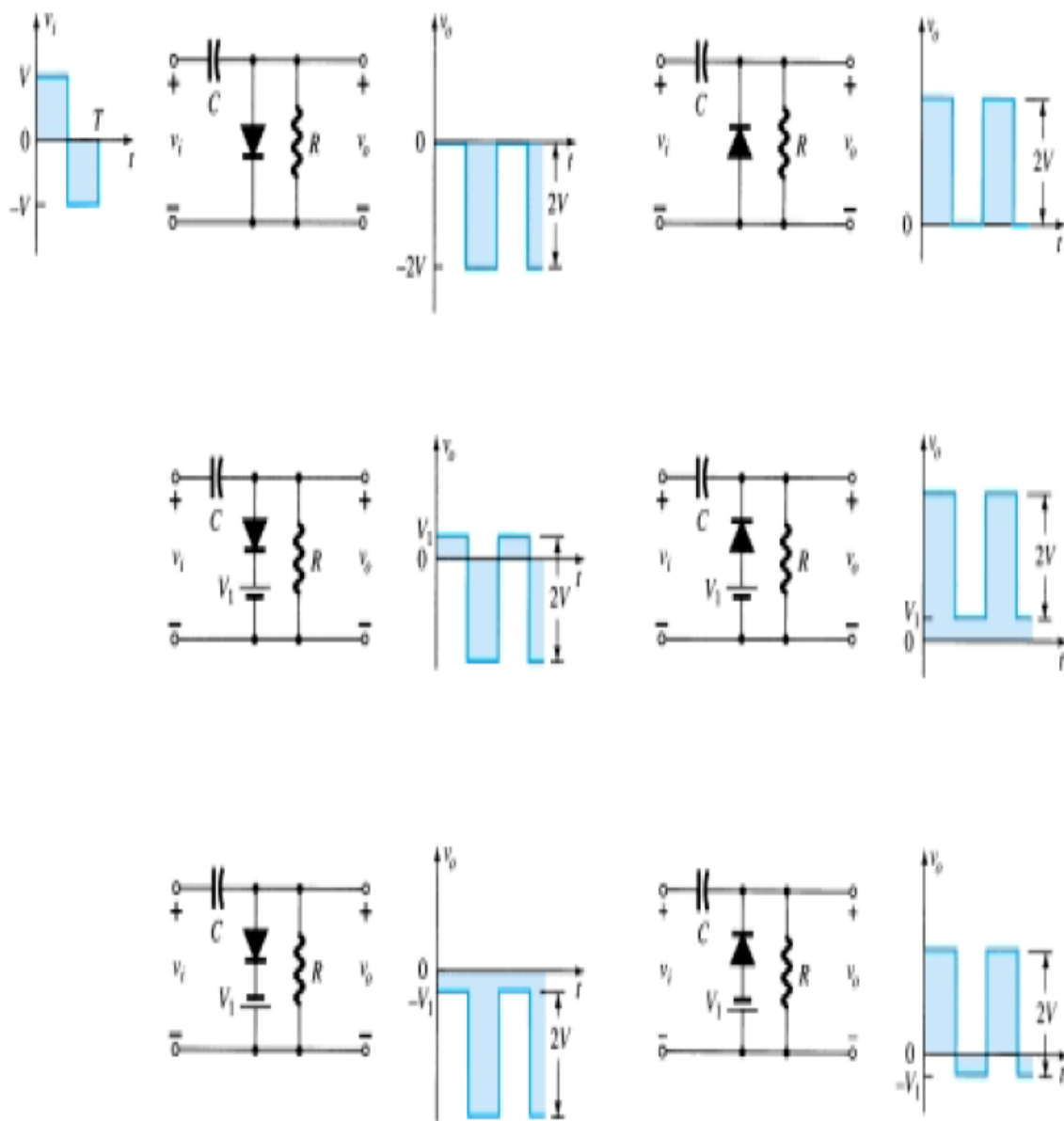


Figure 2.103 Clamping circuits with ideal diodes ($5\tau = 5RC \gg T/2$).

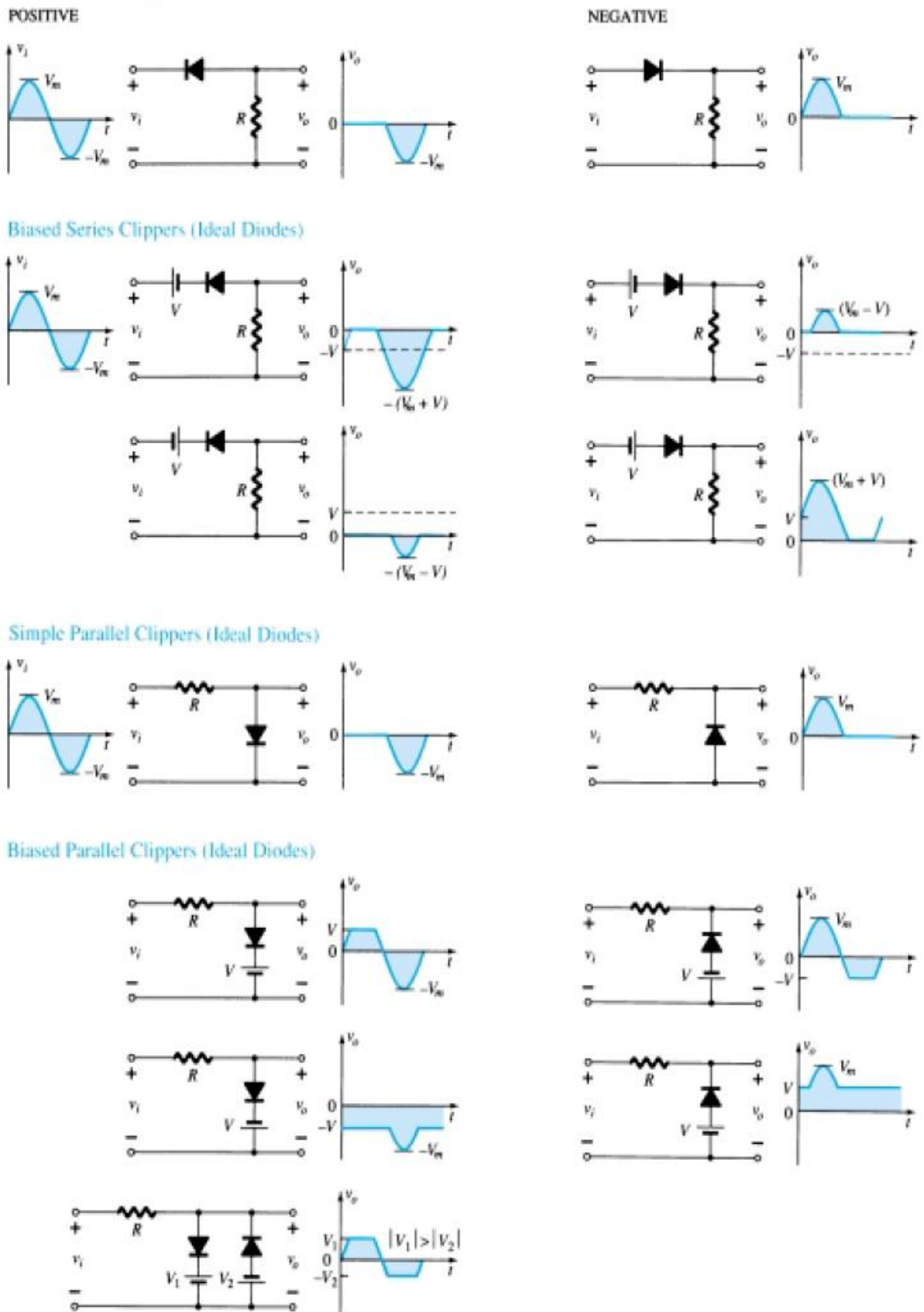


Figure 2.91 Clipping circuits.